

PhysicsByAaryan

CSIR NET . GATE . JEST . BARC - Physics

Basic Electronics - CSIR NET Physics PYQs

Electronics . All PYQs (2015-2025) with answer key

4 questions . Answer key included

www.physicsbyaaryan.com . www.csirnetphysics.com

Contact: 9501976811





Q1. [Dec 2016] . 3.5 marks

Electronics > Basic Electronics

| | | |
|----------|----------|------|
| CSIR NET | 2016 Dec | 3.5M |
|----------|----------|------|

The $I - V$ characteristics of a device is

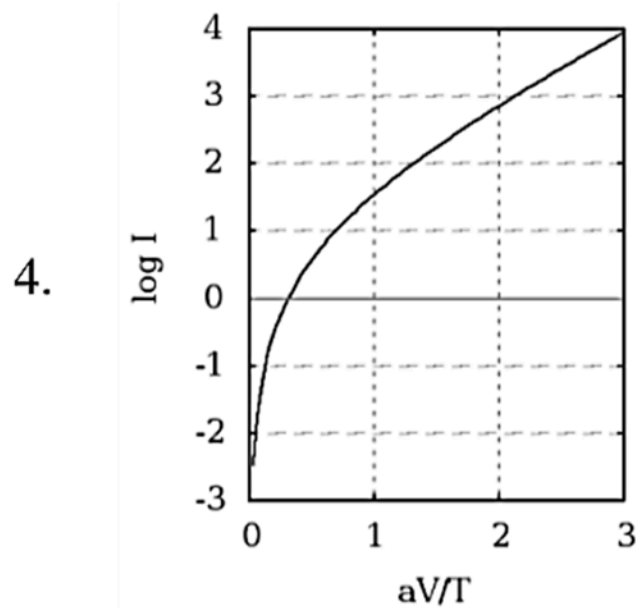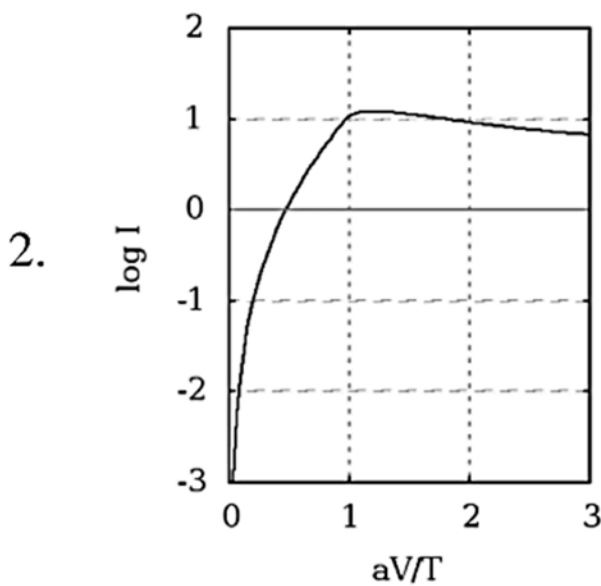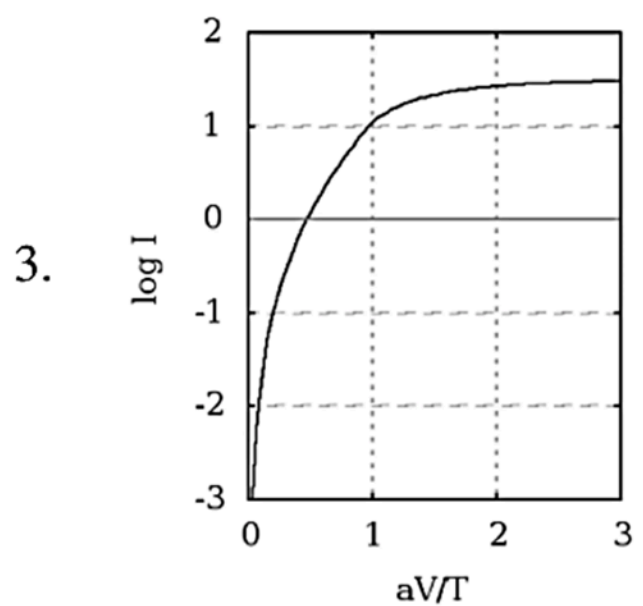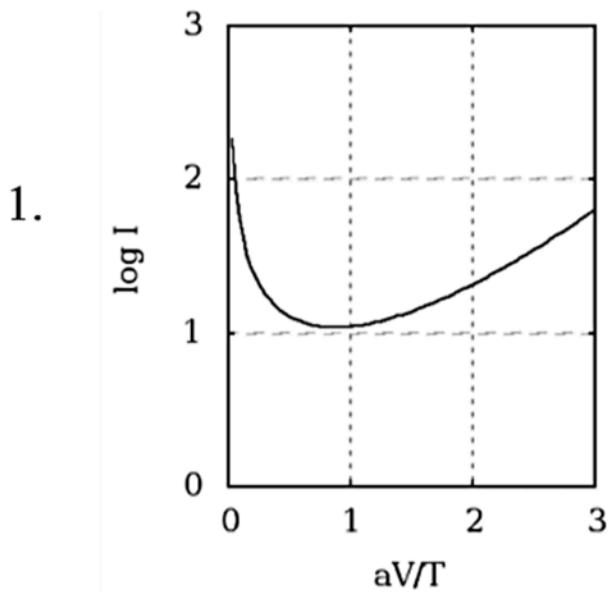$I = I_s \left[\exp\left(\frac{aV}{T}\right) - 1 \right]$, where T is the temperature and a and I_s are constants independent of T and V . Which one of the following plots is correct for a fixed applied voltage V ?



Q2. [June 2016] . 3.5 marks

Electronics > Basic Electronics

| | | |
|----------|-----------|------|
| CSIR NET | 2016 June | 3.5M |
|----------|-----------|------|

The dependence of current I on the voltage V of a certain device is given by

$$I = I_0 \left(1 - \frac{V}{V_0} \right)^2$$

where I_0 and V_0 are constants. In an experiment the current I is measured as the voltage V applied across the device is increased. The parameters V_0 and $\sqrt{I_0}$ can be graphically determined as


1. the slope and the y -intercept of the $I - V^2$ graph
2. the negative of the ratio of the y -intercept and the slope, and the y -intercept of the $I - V^2$ graph
3. the slope and the y -intercept of the $\sqrt{I} - V$ graph
4. the negative of the ratio of the y -intercept and the slope, and the y -intercept of the $\sqrt{I} - V$ graph

Q3. [Dec 2024] . 3.5 marks

Electronics > Basic Electronics


| | | |
|-----------------|-----------------|-------------|
| CSIR NET | 2024 Dec | 3.5M |
|-----------------|-----------------|-------------|

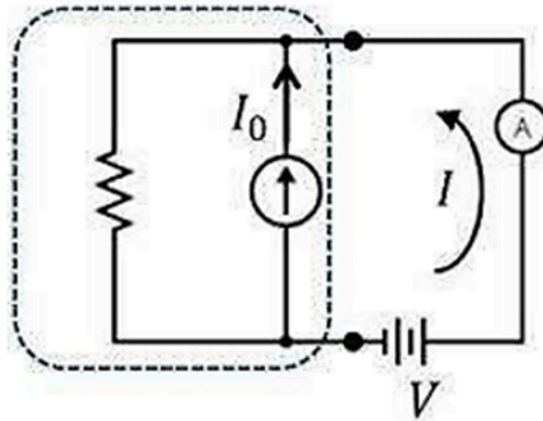A circuit component consists of a resistor in parallel with an ideal current source. The I-V characteristics of the component was measured using a variable voltage source and an ammeter 'A' :




The arrow in the figure indicates the positive direction of current. The I-V characteristics of the component is best represented by


1.

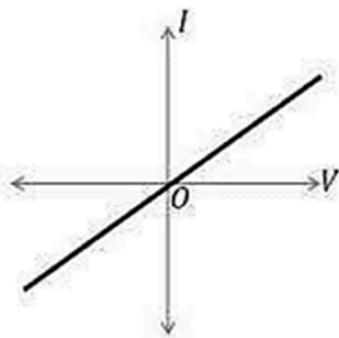


2.

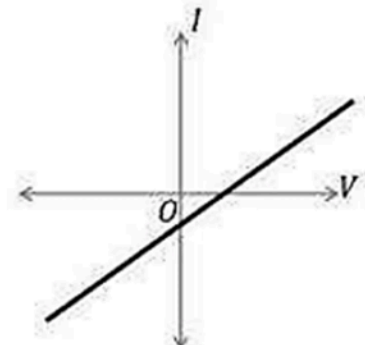

3.

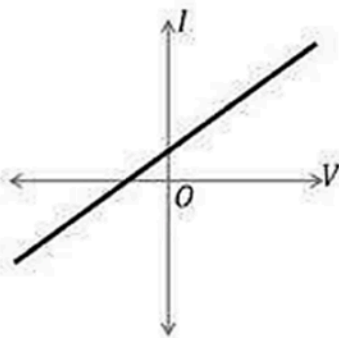

4.

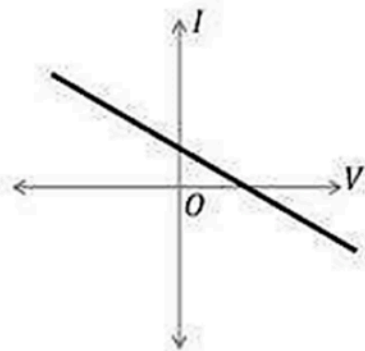

Q4. [June 2024] . 5.0 marks

Electronics > Basic Electronics


CSIR NET

2024 June

5M

In the circuit shown in the figure, the resistances R and R' change due to strain. While R increases, R' decreases by the same amount ΔR due to the applied strain. The unstrained values of R and R' are 100Ω each. If same strain is applied to all the resistors, and the output voltage (V_{ab}) changes to 0.3 V , then ΔR is closest to

1. 3Ω
2. 1.5Ω
3. 4.5Ω
4. 6Ω

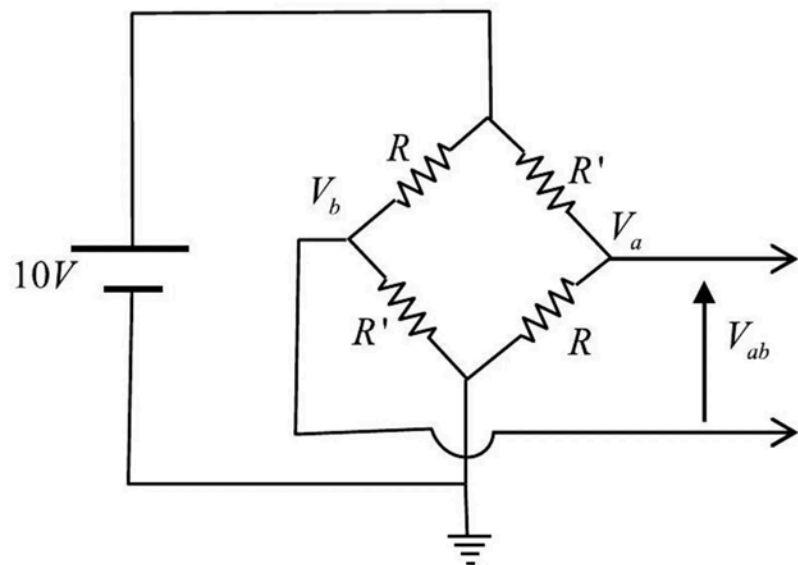

Answer Key

4 questions . Subject and topic for quick revision

| Q. No | Subject | Topic | Answer |
|-------|-------------|-------------------|--------|
| Q1 | Electronics | Basic Electronics | 4 |
| Q2 | Electronics | Basic Electronics | 4 |
| Q3 | Electronics | Basic Electronics | 2 |
| Q4 | Electronics | Basic Electronics | 1 |

Study with PhysicsByAaryan

Full CSIR NET / GATE / JEST / BARC Physics live batch by Aaryan Mehra Sir.
Concept-first teaching, complete PYQ coverage, daily doubt support.

Use coupon CONSISTENCY for Rs. 500 off

Visit

www.physicsbyaaryan.com

www.csirnetphysics.com

Contact

9501976811