

# PhysicsByAaryan

CSIR NET . GATE . JEST . BARC - Physics

## FET - CSIR NET Physics PYQs

Electronics . All PYQs (2015-2025) with answer key

**4 questions . Answer key included**

---

[www.physicsbyaaryan.com](http://www.physicsbyaaryan.com) . [www.csirnetphysics.com](http://www.csirnetphysics.com)


Contact: 9501976811

Q1. [Dec 2015] . 5.0 marks

Electronics &gt; FET

CSIR NET	2015 Dec	5 M
----------	----------	-----

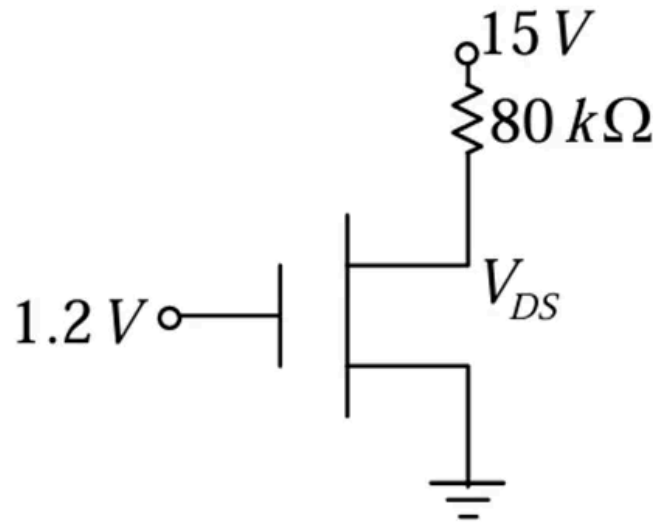Consider an  $n$  - MOSFET with the following parameters: current drive strength  $K = 60\mu A/V^2$ , breakdown voltage  $BV_{DS} = 10 V$ , ratio of effective gate width to the channel length  $\frac{W}{L} = 5$  and threshold voltage  $V_{th} = 0.5 V$ . In the circuit given below, this  $n$ -MOSFET is operating in the





1. ohmic region
2. cut-off region
3. saturation region
4. breakdown

**Q2. [June 2015] . 5.0 marks**





Electronics > FET

<b>CSIR NET</b>	<b>2015 June</b>	<b>5 M</b>
-----------------	------------------	------------

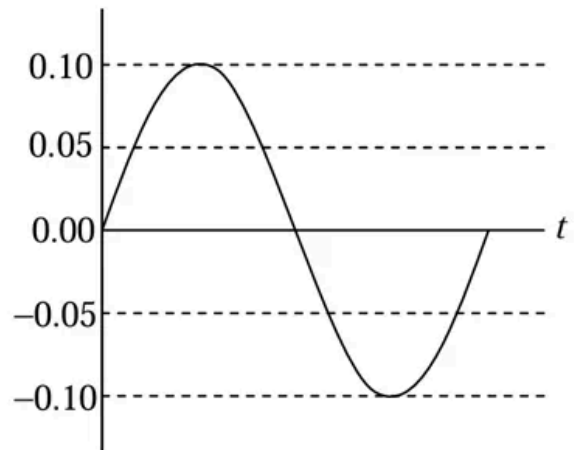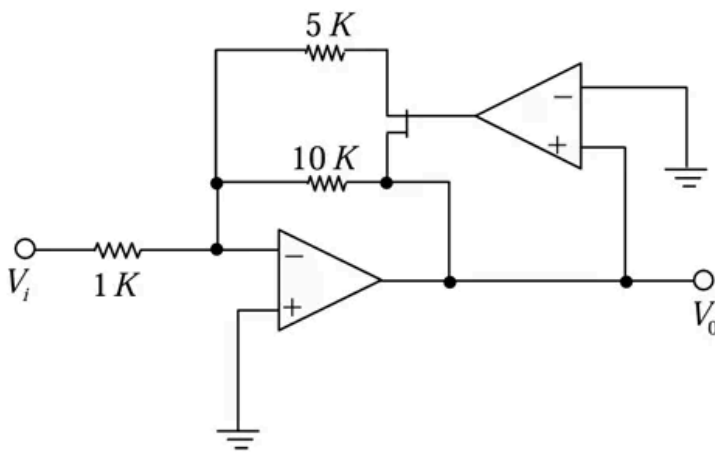For the circuit and the input sinusoidal waveform shown in the figures below, which is the correct waveform at the output?



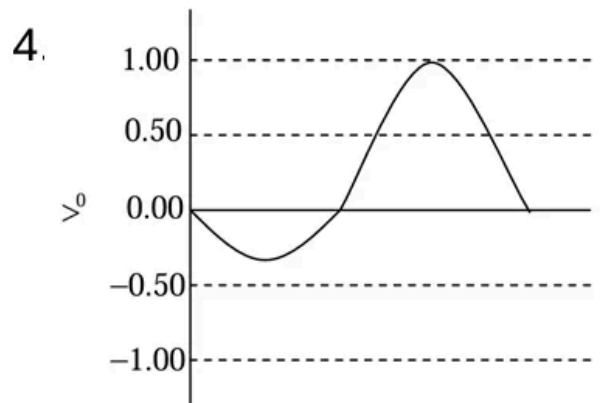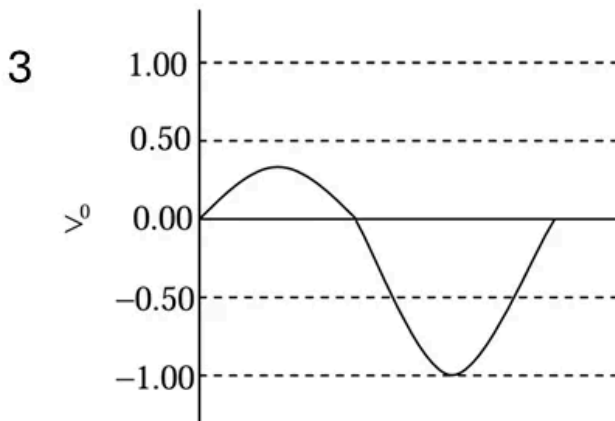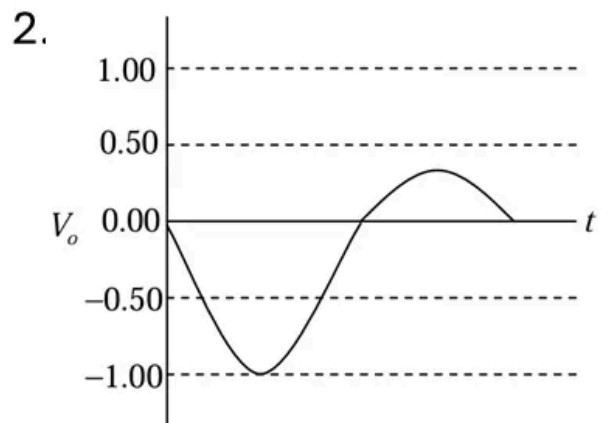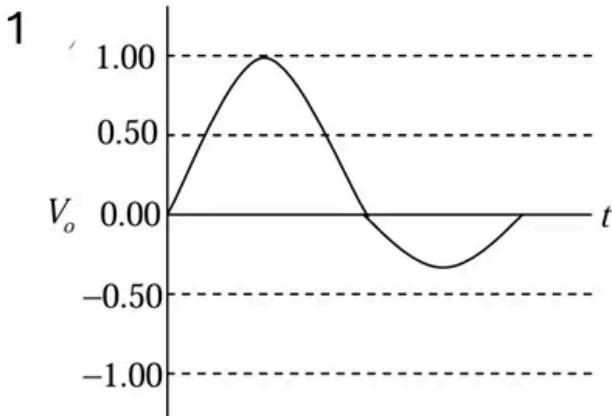(The time scales in all plots are the same.)




## Q3. [June 2017] . 3.5 marks

Electronics &gt; FET

CSIR NET	2017 June	3.5M
----------	-----------	------

In the  $n$ -channel JFET shown in figure below,  $V_i = -2V$ ,  $C = 10pF$ ,  $V_{DD} = +16V$  and  $R_D = 2k\Omega$ . If the drain  $D$  - source  $S$  saturation current  $I_{DSS}$  is  $10mA$  and the pinch-off voltage  $V_P$  is  $-8V$ , then the voltage across points  $D$  and  $S$  is

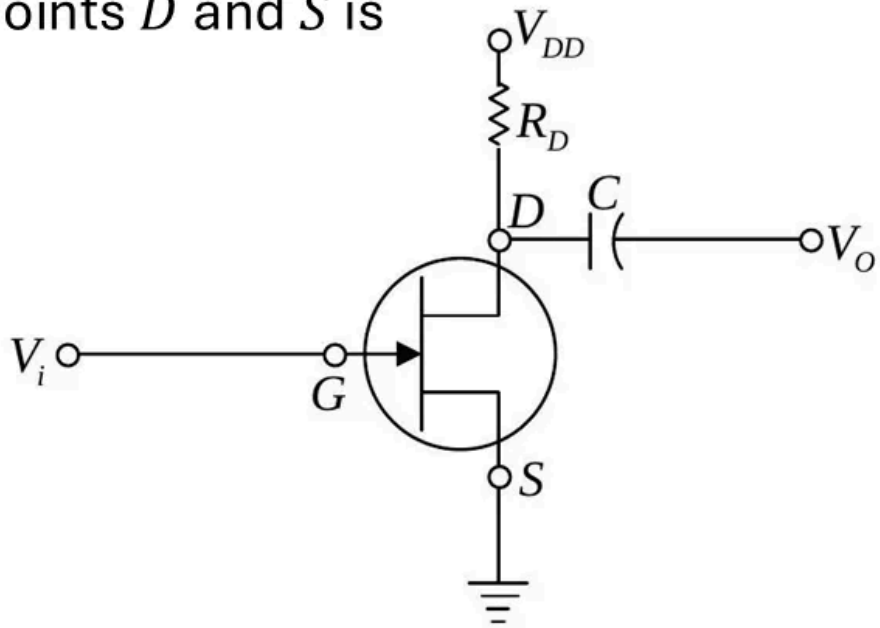1. 11.125 V
2. 10.375 V
3. 5.75 V
4. 4.75 V



Q4. [June 2022] . 3.5 marks

Electronics > FET


CSIR NET

2022 June

3.5M

The circuit containing two n-channel MOSFETs shown below, works as

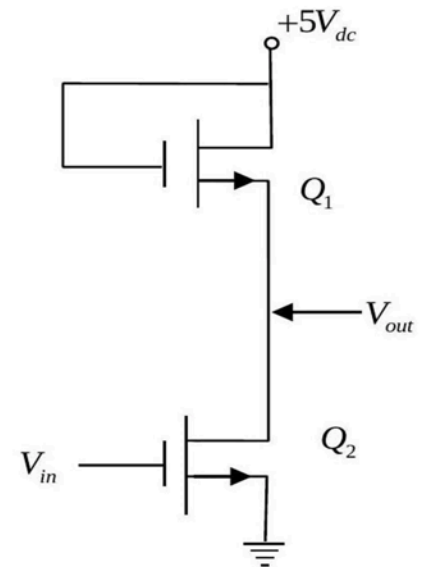1. a buffer
2. a non-inverting amplifier
3. an inverter
4. a rectifier



## Answer Key

4 questions . Subject and topic for quick revision

Q. No	Subject	Topic	Answer
Q1	Electronics	FET	3
Q2	Electronics	FET	2
Q3	Electronics	FET	4
Q4	Electronics	FET	3

# Study with PhysicsByAaryan

---

Full CSIR NET / GATE / JEST / BARC Physics live batch by Aaryan Mehra Sir.  
Concept-first teaching, complete PYQ coverage, daily doubt support.

**Use coupon CONSISTENCY for Rs. 500 off**

## Visit

[www.physicsbyaaryan.com](http://www.physicsbyaaryan.com)

[www.csirnetphysics.com](http://www.csirnetphysics.com)

## Contact

9501976811